

the parts and what they do:

the **attiny85** is the brains of the circuit...




...it can be programmed and sense/act on things.

**diodes** only allow electricity to go one-way...





...they can only be placed in one direction.


**resistors** are like faucets...

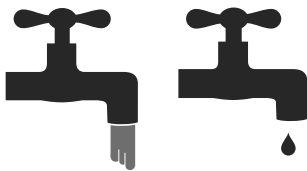


...they can reduce the amount of flow.

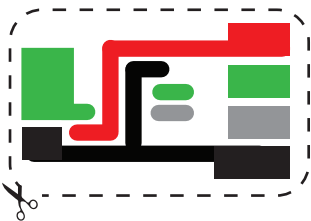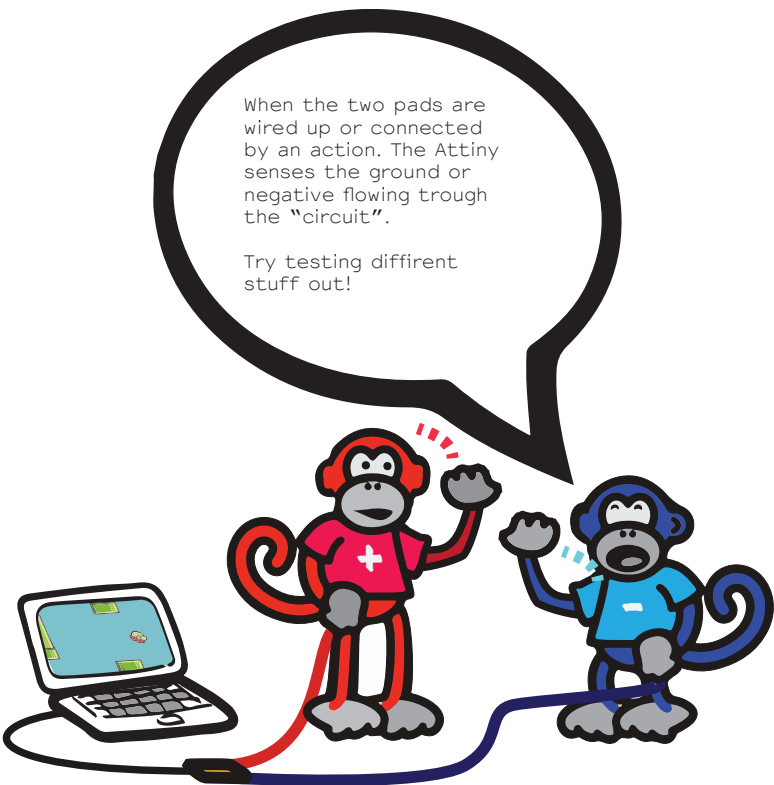


walk through:

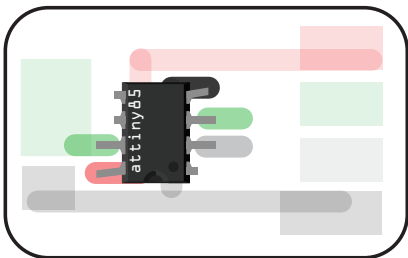




attiny85

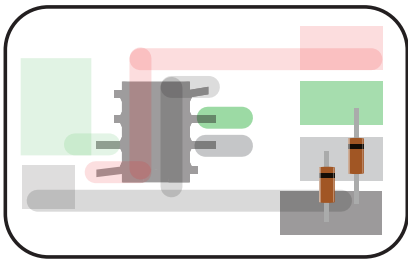

diodes

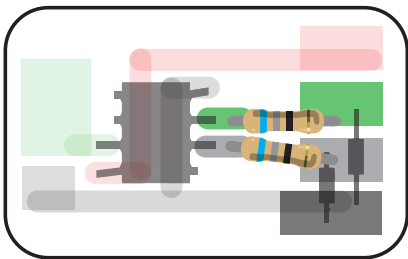


resistors

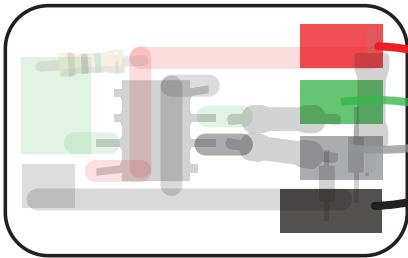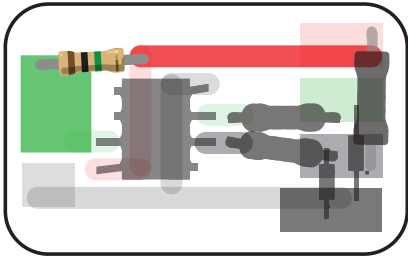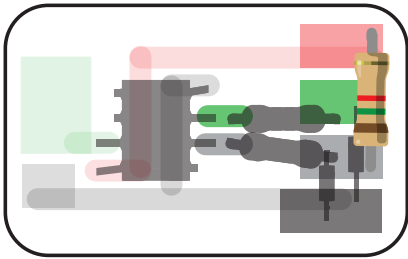


red (+)  
green/blue  
white  
black (-)

usb cable

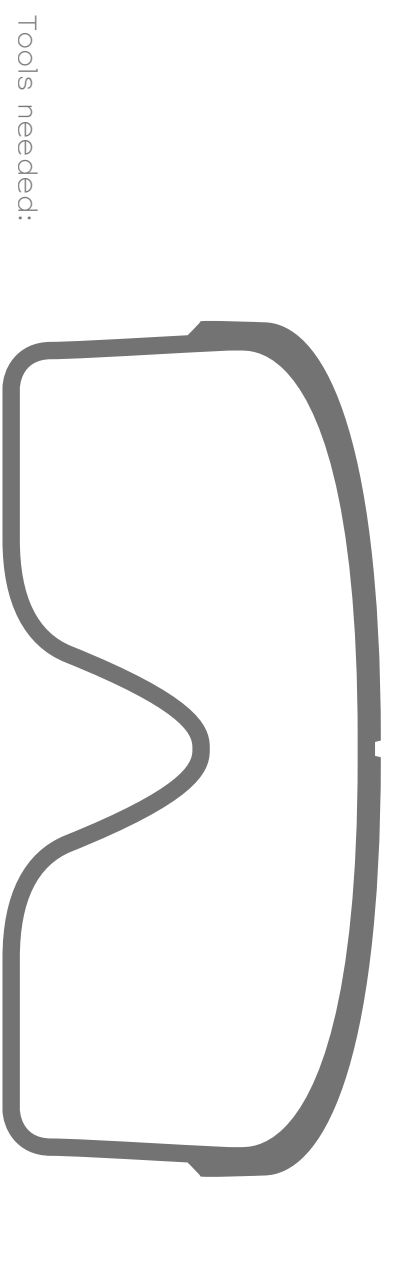

Tools needed:

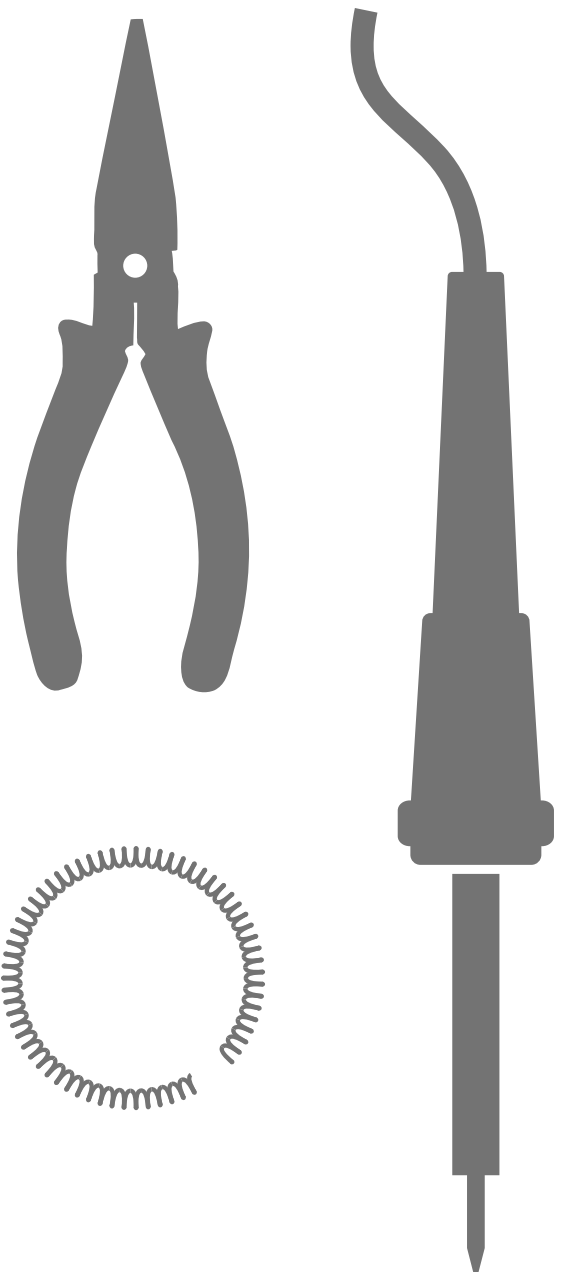

# JawnWare v1:

A low-cost one-key Makey Makey derivative.